

(c) : For forward biased diode, p is at higher potential and n is at lower potential.

For reverse biased diode, p is at lower potential and n is at higher potential.

So, B, C and E is in forward bias.